



# Logic Project

---

**project Name:**

BCD(8421) to/from Excess-3

**Team:**

**section 6**

**Mahmoud Ezzat El-agami**

**Nada Hashem Mohamed**

**Mostafa Eslam Jeweily**

**Yossef Samy El-Beheiry**

**Mostafa Ezz**

# project Overview

Excess-3 binary code is an **unweighted self-complementary** BCD code.

Self-Complementary property means that the 1's complement of an excess-3 number is the excess-3 code of the 9's complement of the corresponding decimal number. This property is useful since a decimal number can be nines' complemented (for subtraction) as easily as a binary number can be ones' complemented; just by inverting all bits.

For example, the excess-3 code for 3(0011) is 0110, and to find the excess-3 code of the complement of 3, we just need to find the 1's complement of 0110  $\rightarrow$  1001, which is also the excess-3 code for the 9's complement of 3  $\rightarrow$   $(9-3) = 6$ .

# Converting BCD (8421) to Excess -3-


As is clear by the name, a BCD digit can be converted to its corresponding Excess-3 code by simply adding 3 to it. Since we have only 10 digits(0 to 9) in decimal, we don't care about the rest and marked them with a cross( X ).

Let  $A, B, C$  and  $D$  be the bits representing the binary numbers, where  $A$  is the LSB and  $D$  is the MSB, and Let  $w, x, y$  and  $z$  be the bits representing the gray code of the binary numbers, where  $w$  is the LSB and  $z$  is the MSB.

The truth table for the conversion is given below. The X's mark is don't care condition.

BCD(8421)				Excess-3			
A	B	C	D	w	x	y	z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

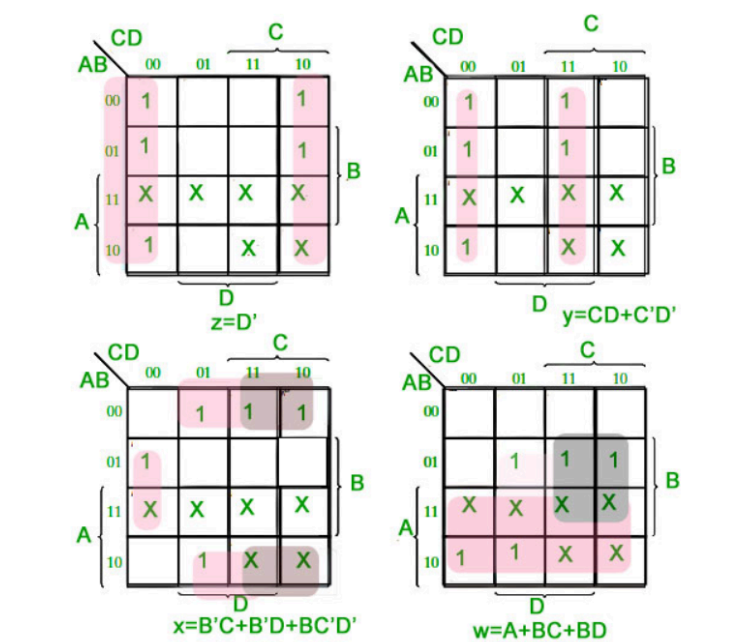To find the corresponding digital circuit, we will use the K-Map technique for each of the Excess-3 code bits as output with all of the bits of the BCD number as input.



Corresponding minimized Boolean expressions for Excess-3 code bits –


$$w = A + BC + BD$$

$$x = B'C + B'D + BC'D'$$

$$y = CD + C'D'$$

$$z = D'$$

The corresponding digital circuit-

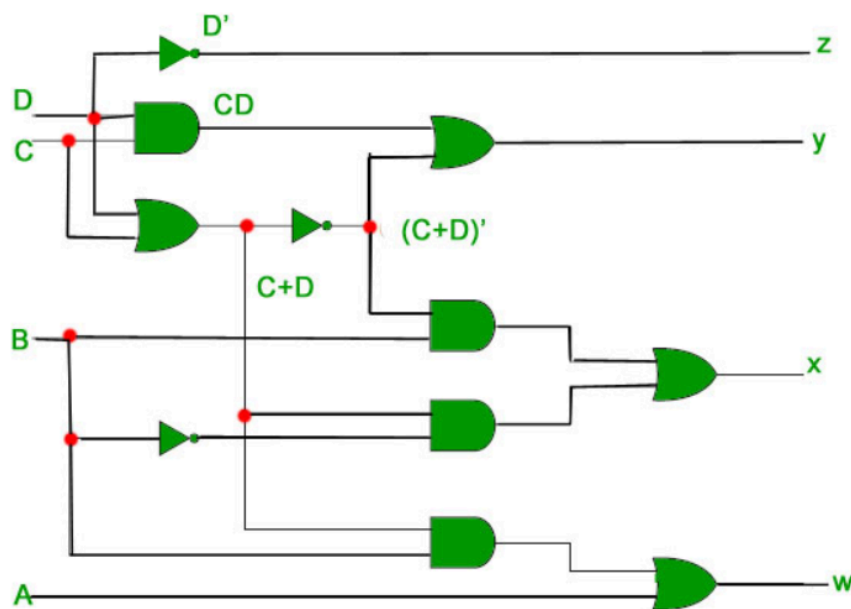

# Converting Excess -3- to BCD (8421)-

Excess-3 code can be converted back to BCD in the same manner.

Let  $A, B, C$  and  $D$  be the bits representing the binary numbers, where  $D$  is the LSB and  $A$  is the MSB, and

Let  $w, x, y$  and  $z$  be the bits representing the gray code of the binary numbers, where  $D$  is the LSB and  $w$  is the MSB.

The truth table for the conversion is given below. The X's mark is don't care condition.

Excess-3				BCD			
w	x	y	z	A	B	C	D
0	0	0	0	X	X	X	X
0	0	0	1	X	X	X	X
0	0	1	0	X	X	X	X
0	0	1	1	0	0	0	0
0	1	0	0	0	0	0	1
0	1	0	1	0	0	1	0
0	1	1	0	0	0	1	1
0	1	1	1	0	1	0	0
1	0	0	0	0	1	0	1
1	0	0	1	0	1	1	0
1	0	1	0	0	1	1	1
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	1
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

**K-Map for D-**



wx \ yz	00	01	11	10
00	X	X	0	X
01	1	0	0	1
11	1	X	X	X
10	1	0	0	1

## K-Map for C-

wx \ yz	00	01	11	10
00	X	X	0	X
01	0	1	0	1
11	0	X	X	X
10	0	1	0	1

## K-Map for B-

wx \ yz	00	01	11	10
00	X	X	0	X
01	0	0	1	0
11	0	X	X	X
10	1	1	0	1

# K-Map for A-

		yz			
		00	01	11	10
wx	00	X	X	0	X
	01	0	0	0	0
	11	1	X	X	X
	10	0	0	1	0

Corresponding minimized boolean expressions for Excess-3 code bits –

$$A = wx + wyz$$

$$B = x'y' + x'z' + xyz$$

$$C = y'z + yz'$$

$$D = z'$$

The corresponding digital circuit –

Here E3, E2, E1 and E0 correspond to w, x, y and z and B3, B2, B1 and B0 correspond to A, B, C and D

